

Inrush-current limitor, short cirquit on sec. side

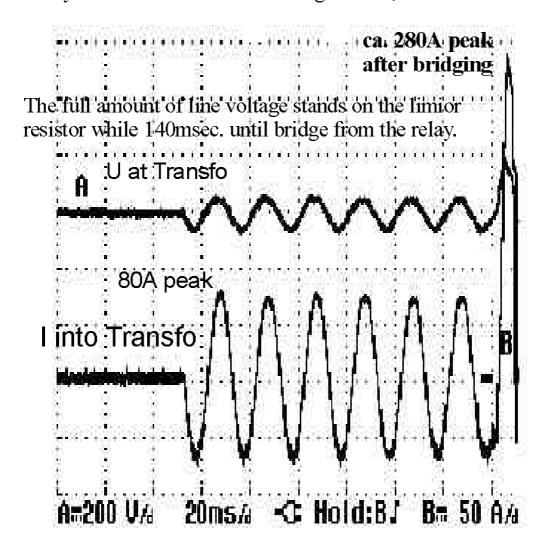2 kVA Toroid Transformer with secondary side short cirquit switch on with ordinary Inrush current limitor for 230V 16A. Fused with 16A C-Typ cirquit breaker, who trips when the relays in the current limitor bridges the 3,5 Ohm resistor.



the limitor was damaged with this switching on a short cirquit. The C16A cirquit breaker trips after bridging. To late to protect the resistor.

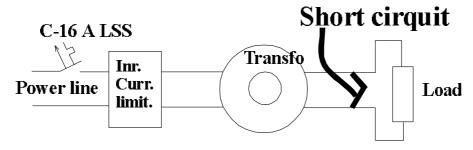The relays in the limitor could no more bridge at the next switching and the resistor has burned.



esbkzschle.cdr, ESB-on shortcirquit1e.cdr